



Conclusion:

Hence, the solution of differential equation is the $V(a)$. The eqn can be successfully solved using three op-amps. The transient analysis shows the solution of our diff. equation:

